

实验报告 基于Verilog和FPGA/CPLD的多功能秒表设计

- 学号: 516202910010
- 姓名: 邓公清

实验目的

1. 初步掌握利用Verilog硬件描述语言进行逻辑功能设计的原理和方法。
2. 理解和掌握运用大规模可编程逻辑器件进行逻辑设计的原理和方法。
3. 理解硬件实现方法中的并行性，联系软件实现方法中的并发性。
4. 理解硬件和软件是相辅相成、并在设计 and 应用方法上的优势互补的特点。

实验内容和任务

1. 运用Verilog硬件描述语言，基于DE1-SOC实验板，设计实现一个具有较多功能的计时秒表。
2. 要求将6个数码管设计为具有“分：秒：毫秒”显示，按键的控制动作有：“计时复位”、“计数/暂停”、“显示暂停/显示继续”等，功能能够满足马拉松或长跑运动员的计时需要。
3. 利用示波器观察按键的抖动，设计按键电路的消抖方法。
4. 在实验报告中详细报告自己的设计过程、步骤及Verilog代码。


实验仪器

1. 硬件：DE1-SoC实验板
2. 软件：Altera Quartus II 13.1 Web Edition

实验过程

1. 以指导书上的代码模版为基础，结合实验要求进行分析设计。
2. 建立工程，结合官方文档编写并调试项目，编译得到目标程序。
3. 将目标程序写入实验板，进行最后的调试。

顶层设计

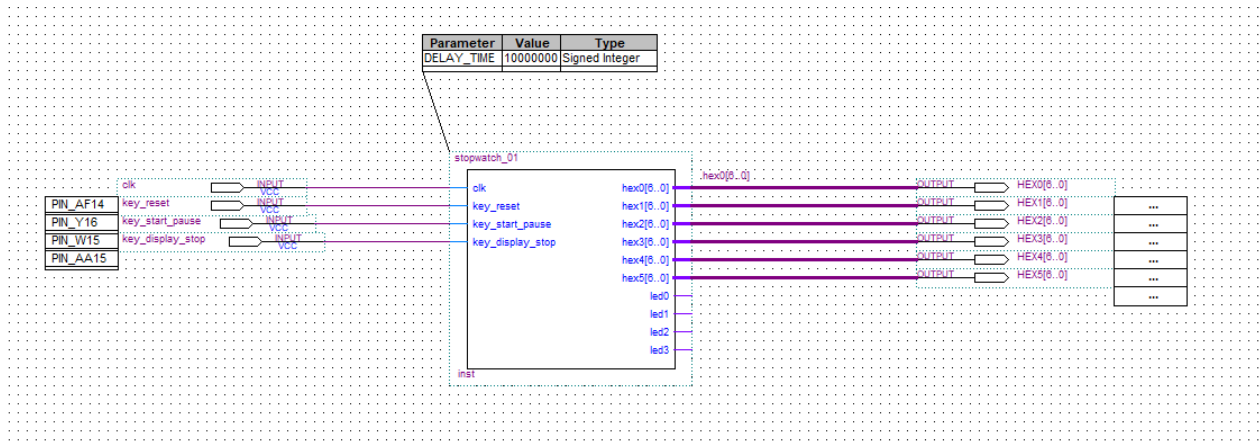

- 输入为接入板载50MHz的时钟和三个按键。
- 输出为6个7段管的7bit二进制值。
- 秒表完整逻辑全部包含于stopwatch_01模块中。

主要代码

```
module stopwatch_01(clk,key_reset,key_start_pause,key_display_stop,
                    hex0,hex1,hex2,hex3,hex4,hex5,
                    led0,led1,led2,led3);
    input  clk,key_reset,key_start_pause,key_display_stop;
    output [6:0] hex0,hex1,hex2,hex3,hex4,hex5;
    output led0,led1,led2,led3;
    reg led0,led1,led2,led3;

    reg display_work;
    reg counter_work;

    parameter DELAY_TIME = 10000000;

    reg [3:0] minute_display_high;
    reg [3:0] minute_display_low;
    reg [3:0] second_display_high;
    reg [3:0] second_display_low;
    reg [3:0] msecond_display_high;
    reg [3:0] msecond_display_low;

    reg [3:0] minute_counter_high;
    reg [3:0] minute_counter_low;
    reg [3:0] second_counter_high;
    reg [3:0] second_counter_low;
    reg [3:0] msecond_counter_high;
    reg [3:0] msecond_counter_low;

    reg [31:0] counter_50M;

    reg reset_1_time;
    reg [31:0] counter_reset;
```

```

reg start_1_time;
reg [31:0] counter_start;
reg display_1_time;
reg [31:0] counter_display;

reg start;
reg display;

sevensseg LED8_minute_display_high(minute_display_high,hex5);
sevensseg LED8_minute_display_low(minute_display_low,hex4);
sevensseg LED8_second_display_high(second_display_high,hex3);
sevensseg LED8_second_display_low(second_display_low,hex2);
sevensseg LED8_msecond_display_high(msecond_display_high,hex1);
sevensseg LED8_msecond_display_low(msecond_display_low,hex0);

initial
begin
    display_work = 0;
    counter_work = 0;

    minute_display_high = 0;
    minute_display_low = 0;
    second_display_high = 0;
    second_display_low = 0;
    msecond_display_high = 0;
    msecond_display_low = 0;

    minute_counter_high = 0;
    minute_counter_low = 0;
    second_counter_high = 0;
    second_counter_low = 0;
    msecond_counter_high = 0;
    msecond_counter_low = 0;

    counter_50M = 0;

    reset_1_time = 0;
    counter_reset = 0;
    start_1_time = 0;
    counter_start = 0;
    display_1_time = 0;
    counter_display = 0;

    start = 0;
    display = 0;
end

// process with input and display at each clk posedge
always@(posedge clk)

```

```

begin

    // increase the minimal counter when counter_work is true
    if(counter_work)counter_50M = counter_50M + 1;

    // update LEDs when display_work is true
    if(display_work)
    begin
        minute_display_high = minute_counter_high;
        minute_display_low  = minute_counter_low;
        second_display_high = second_counter_high;
        second_display_low  = second_counter_low;
        msecond_display_high = msecond_counter_high;
        msecond_display_low  = msecond_counter_low;
    end

    // check input with joggle removing
    // it looks like triggering on the button pressed down rather up
    if(!key_display_stop && !counter_display)counter_display = 1;
    if(counter_display)counter_display = counter_display + 1;
    if(!key_reset && !counter_reset)counter_reset = 1;
    if(counter_reset)counter_reset = counter_reset + 1;
    if(!key_start_pause&& !counter_start)counter_start = 1;
    if(counter_start)counter_start = counter_start + 1;

    if(counter_reset == DELAY_TIME)
    begin
        minute_display_high = 0;
        minute_display_low = 0;
        second_display_high = 0;
        second_display_low = 0;
        msecond_display_high = 0;
        msecond_display_low = 0;

        minute_counter_high = 0;
        minute_counter_low = 0;
        second_counter_high = 0;
        second_counter_low = 0;
        msecond_counter_high = 0;
        msecond_counter_low = 0;

        counter_50M = 0;
    end

    if(counter_display == DELAY_TIME)
    begin
        counter_display = 0;
        display_work = !display_work;
    end
end

```

```

if(counter_start == DELAY_TIME)
begin
    counter_start = 0;
    counter_work = !counter_work;
end

// process counter
if(counter_50M == 500000)
begin
    counter_50M = 0;
    msecond_counter_low = msecond_counter_low + 1;

    if(msecond_counter_low == 10)
    begin
        msecond_counter_high = msecond_counter_high + 1;
        msecond_counter_low = 0;
    end

    if(msecond_counter_high == 10)
    begin
        second_counter_low = second_counter_low + 1;
        msecond_counter_high = 0;
    end

    if(second_counter_low == 10)
    begin
        second_counter_high = second_counter_high + 1;
        second_counter_low = 0;
    end

    if(second_counter_high == 6)
    begin
        minute_counter_low = minute_counter_low + 1;
        second_counter_high = 0;
    end

    if(minute_counter_low == 10)
    begin
        minute_counter_high = minute_counter_high + 1;
        minute_counter_low = 0;
    end

    if(minute_counter_high == 10)
    begin
        minute_counter_high = 0;
    end
end
end
end

```

```

endmodule

module sevenseg(data,ledsegments);
    input [3:0] data;
    output ledsegments;
    reg [6:0] ledsegments;

    always@(*)
    case(data)
        0:ledsegments = 7'b100_0000;
        1:ledsegments = 7'b111_1001;
        2:ledsegments = 7'b010_0100;
        3:ledsegments = 7'b011_0000;
        4:ledsegments = 7'b001_1001;
        5:ledsegments = 7'b001_0010;
        6:ledsegments = 7'b000_0010;
        7:ledsegments = 7'b111_1000;
        8:ledsegments = 7'b000_0000;
        9:ledsegments = 7'b001_0000;
        default:ledsegments = 7'b111_1111;
    endcase
endmodule

```

消除抖动

```

// check input with joggle removing
// it looks like triggering on the button pressed down rather up
if(!key_display_stop && !counter_display)counter_display = 1;
if(counter_display)counter_display = counter_display + 1;
if(!key_reset && !counter_reset)counter_reset = 1;
if(counter_reset)counter_reset = counter_reset + 1;
if(!key_start_pause&& !counter_start)counter_start = 1;
if(counter_start)counter_start = counter_start + 1;

if(counter_reset == DELAY_TIME) ...
if(counter_display == DELAY_TIME) ...
if(counter_start == DELAY_TIME) ...

```

一个能够保证长按的幂等判断和延时触发逻辑。

十进制转换为七段管信号

```

module sevenseg(data,ledsegments);
    input [3:0] data;
    output ledsegments;
    reg [6:0] ledsegments;

```

```
always@(*)
case(data)
  0:ledsegments = 7'b100_0000;
  1:ledsegments = 7'b111_1001;
  2:ledsegments = 7'b010_0100;
  3:ledsegments = 7'b011_0000;
  4:ledsegments = 7'b001_1001;
  5:ledsegments = 7'b001_0010;
  6:ledsegments = 7'b000_0010;
  7:ledsegments = 7'b111_1000;
  8:ledsegments = 7'b000_0000;
  9:ledsegments = 7'b001_0000;
  default:ledsegments = 7'b111_1111;
endcase
endmodule
```

实验总结

1. 在实践中消抖操作极为重要，原因如下：
 1. 消除因实验板接触问题而导致的实验板逻辑错误。
 2. 保证按钮触发的逻辑正确性。
 3. 防止误触。
2. 实验中需要频繁查询实验板的相关文档和参考，完成实验的过程包含了大量编码以外的操作，熟练的查询文档和使用Quartus II软件变得极为重要。
3. 实验包含了代码部分和相关的硬件部分，让我进一步明白到了软硬件如何相互协调工作。